

# CS 121: Lecture 6

## Code = Data

Madhu Sudan

<https://madhu.seas.harvard.edu/courses/Fall2020>

Book: <https://introtcs.org>

How to contact us { The whole staff (faster response): [CS 121 Piazza](#)  
Only the course heads (slower): [cs121.fall2020.course.heads@gmail.com](mailto:cs121.fall2020.course.heads@gmail.com)

# Where we are:

- Definition of Circuits
- Universality of NAND
- All functions can be computed
- $\forall f: \{0,1\}^n \rightarrow \{0,1\}: \text{Size}(f) \leq O\left(\frac{2^n}{n}\right)$
- Claimed:  $\exists f, \text{Size}(f) \geq \Omega\left(\frac{2^n}{n}\right)$
- Today: Will prove above.
- Show: Code = Data
- Show how to interpret Data as Code.

Part I: Circuits:  
Finite computation,  
quantitative study

Part II: Automata:  
Infinite restricted computation,  
quantitative study

Part III: Turing Machines:  
Infinite computation, qualitative study

Part IV: Efficient Computation:  
Infinite computation, quantitative study

Part V: Randomized computation:  
Extending studies to non-classical algorithms

# Today: Code as Data

- Circuits can be represented by bits
- Exercise break: Quantify above. Prove lower bound on Circuit size (for hardest function).
- Universality: Circuit Interpreter  $I(C,x) = C(x)$ 
  - As immediate consequence of "Code as data" - Inefficient
- Efficient Circuit Interpreter (sketch)
- Exercise break: Some Ingredients


# Notation: $\text{SIZE}(s)$

Answer was: The circuit is not in  $\text{SIZE}(\text{anything})$  since circuits are not functions. Underlying function is in  $\text{SIZE}(1)$ .

- $\text{SIZE}(s) = \{f: \{0,1\}^n \rightarrow \{0,1\} \mid \exists C \text{ with } \leq s \text{ NAND gates computing } f\}$
- $\text{SIZE}(s)$  = Our first complexity class!
  - Always a set (aka "class") of functions, not algorithms!
  - Is the following in  $\text{SIZE}(3)$ ?  $\text{SIZE}(10)$ ?



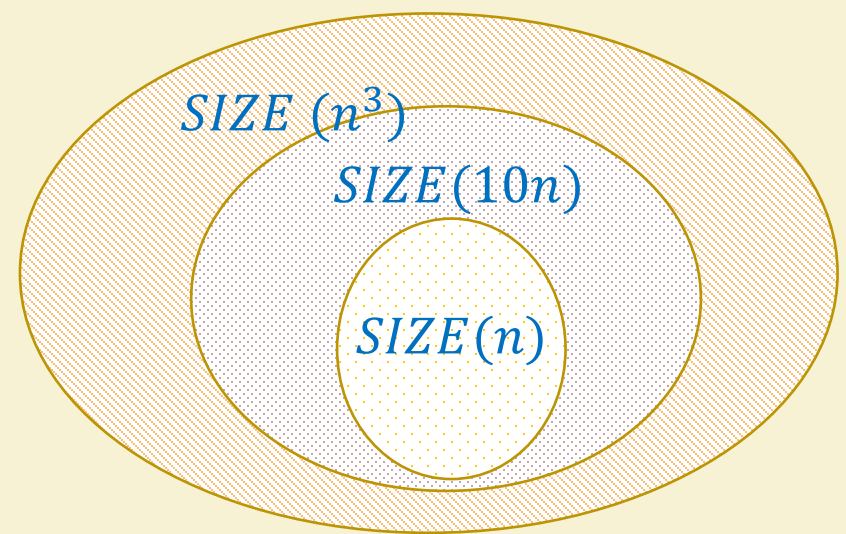- $\text{ALL}_n = \{f: \{0,1\}^n \rightarrow \{0,1\}\}$
- Thm:  $\text{ALL}_n \subseteq \text{SIZE}\left(o\left(\frac{2^n}{n}\right)\right)$
- (Claimed) Thm:  $\text{ALL}_n \not\subseteq \text{SIZE}\left(o\left(\frac{2^n}{n}\right)\right)$



# Reminder: Circuit $\equiv$ Straightline Program

Temp[0]  $\leftarrow$  NAND( $X[0]$ ,  $X[1]$ )

Temp[1]  $\leftarrow$  NAND( $X[2]$ ,  $X[2]$ )

...

Temp[ $i$ ]  $\leftarrow$  NAND(Temp[ $j$ ],  $X[k]$ )

...

$Y[0]$   $\leftarrow$  NAND( $X[0]$ ,  $X[1]$ )

...

$Y[m-1]$   $\leftarrow$  NAND( $X[0]$ ,  $X[1]$ )

Encode to  $\{0,1\}^*$  in class

$(0 \leftarrow \overline{X_0, X_1})$

$(1 \leftarrow X_2, X_2)$

$(i \leftarrow T_j, X_k)$

$i, j, k \dots \in [n + s]$

$s = \# \text{ lines}$

# Exercise Break 1:


1. Make Representation quantitative:

- Give (prefix-free)  $E: \text{Circuits} \rightarrow \{0,1\}^*$ , such that  $\forall C$  with  $\leq s$  gates,  $|E(C)| = O(s \log s)$

2. Show  $|\mathbf{SIZE}(s)| = 2^{O(s \log s)}$

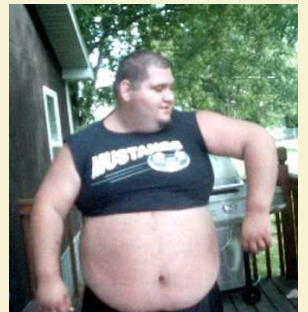3. Show  $\exists f: \{0,1\}^n \rightarrow \{0,1\}$  s.t.  $f \notin \mathbf{SIZE}\left(o\left(\frac{2^n}{n}\right)\right)$   $\left(\Leftrightarrow \mathbf{ALL}_n \notin \mathbf{SIZE}\left(o\left(\frac{2^n}{n}\right)\right)\right)$

Bonus question (0 points):  
Why do Boaz Barak's slides  
associate this picture with  
3<sup>rd</sup> exercise!



# Representation

$S$  gates: Each gate = 3 variables

- represent each line by  
 $3 \log(\cancel{S}) + O(1)$

- total  $S \times 3 \log(\cancel{S}) + O(1)$

Prefix-free  $\rightarrow O(\log S) + \downarrow O(S \log S)$

## Part 1: Representation:

- We represent the circuit as a list of lines.
- So need a prefix-free representation of line.
- line = ordered tuple of 3 variables; Each variable from a set of  $n+s$  variables  $\leq 3s$  variables

$n$  inputs  $\uparrow$   $s$  temp variables  $\uparrow$

[Can use  $n \leq 2s$ , since other inputs not involved in any gate]

$\Rightarrow$  line requires  $3 \log(3s)$  bits.

$\Rightarrow$  Circuit requires  $S \times (\text{bits/per line}) = S \times 3 \log 3s = O(S \log s)$





Part (2):

• Let  $CIRCUIT(S) = \{ \text{all circuits with at most } s \text{ NAND gates} \}$

• We will prove  $|SIZE(S)| \leq |CIRCUIT(S)| \leq | \{0,1\}^{O(s \log s)} |$   
 $= 2^{O(s \log s)}$

• Consider the map  $A: SIZE(S) \rightarrow CIRCUIT(S)$

where given  $f \in SIZE(S)$ ,  $A(f)$  is a circuit of size  $\leq s$  that computes  $f$ .

$A$  is 1-1 since  $A(f) = A(g) \Rightarrow f = g$  [any given circuit computes one function]

$\Rightarrow |SIZE(S)| \leq |CIRCUIT(S)|$

• From Part 1 of Exercise we have  
 $\exists: \text{CIRCUIT}(s) \rightarrow \{0,1\}^{O(s \log s)}$  that is 1-1.

$$\Rightarrow |\text{CIRCUIT}(s)| \leq |\{0,1\}^{O(s \log s)}| = 2^{O(s \log s)}$$

□

For part (3), recall  $\text{ALL}_n = \{f: \{0,1\}^n \rightarrow \{0,1\}\}$   
 $\text{SIZE}(o(\frac{2^n}{n})) = \{f \in \text{ALL}_n \mid f \text{ has circuits of size } o(\frac{2^n}{n})\}$

• We wish to show

$$\text{ALL}_n \not\subseteq \text{SIZE}(o(\frac{2^n}{n})) \left[ \begin{array}{l} \exists f \in \text{ALL}_n \text{ that does} \\ \text{not have } o(\frac{2^n}{n}) \text{ sized} \\ \text{circuits} \end{array} \right]$$

• BIG BODY SMALL SHIRT Principle

if  $|A| > |B|$  then  $A \not\subseteq B$

• Apply to  $A = \text{ALL}_n \Rightarrow |A| = 2^{2^n}$  [can you prove this?]

$$B = \text{SIZE}\left(o\left(\frac{2^n}{n}\right)\right) \Rightarrow |B| = 2^{o\left(\frac{2^n}{n}\right) \cdot \log \frac{2^n}{n}}$$
$$= 2^{o\left(\frac{2^n}{n} \cdot n\right)} = 2^{o(2^n)}$$

So.  $|A| > |B| \Rightarrow A \not\subseteq B$

$\Rightarrow \text{ALL}_n \not\subseteq \text{SIZE}\left(o\left(\frac{2^n}{n}\right)\right)$



# Interpreting Code

- Objective: Show Data representing Code can be interpreted as code.
- Have just shown:  $\exists E: \text{Circuits} \mapsto \text{binary string, 1-to-1}$   
 $C \text{ has } \leq s \text{ NAND Gates} \Rightarrow |E(C)| = O(s \log s)$
- EVAL:  $(E(C), x) \mapsto C(x), \forall C \text{ with } n \text{ inputs}, x \in \{0,1\}^n$ 
  - EVAL is a partial function – why?

$$\text{EVAL}_{m,n} : \{0,1\}^{m+n} \times \{0,1\}^n \rightarrow \{0,1\}$$

- $\text{EVAL}_{m,n}$  = restriction of EVAL to  $E(C) \in \{0,1\}^m, x \in \{0,1\}^n$ 
  - Thm:  $\text{EVAL}_{m,n}$  computed by circuit of size  $O(2^{m+n})$
  - Proof: Obvious!
  - Implication: Power of Code  $\leftrightarrow$  Data-duality!

## REST OF THE LECTURE :

① You should know the theorem being proved  
(theorem 5.10 in text)  
but proof is not necessary (for hw, tests...)  
(you can read the proof if interested!)

② You should read the "Extended Turing Church Thesis (circum version)" & be aware of the Statement + implications.

# Interpreting Circuits Efficiently.

- Goal: Show  $\text{EVAL}_{m,n} \in \text{SIZE} \left( \underbrace{O((m+n)^2 \log^2 n)} \right)$ 
  - Theorem 5.3 in Barak's IntroTCS.
  - Best bound in literature: close to  $O((m+n) \log^2(m+n))$
  - Great, but not "Meta-circular interpreter" (small interpreter that interprets bigger functions).

$m+n$  vs.  $m$

- ignore the difference


- there are only  $2^m$  real inputs

① length of input =  $n$

② length of circuit =  $S$

③ Encoding length =  $m \geq S$


# Sketch of EVAL

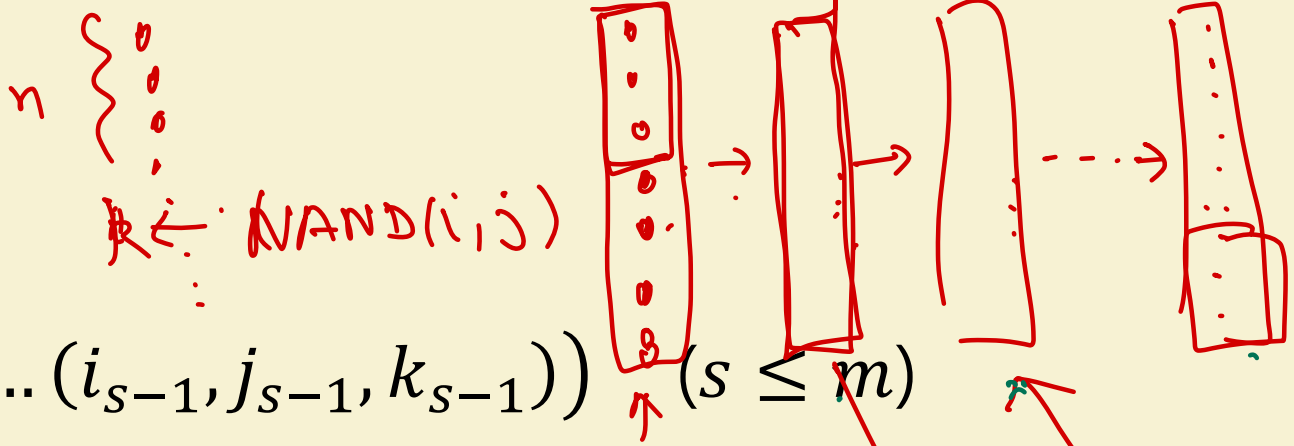

- Recall:  $E(C) = ((i_0, j_0, k_0) \dots (i_{s-1}, j_{s-1}, k_{s-1}))$  ( $s \leq m$ )
- Define:  $W_t \in \{0,1\}^{n+s}$ : Values of  $n$  inputs,  $s$  TEMPs after  $t$  execution steps
- Define:
  - EVAL – ITER:  $(E(C), x, t) \mapsto W_t$
  - EVALHELP:  $(W_{t-1}, i_t, j_t, k_t) \mapsto W_t$  ;
  - EVAL – ITER( $E(C), x, t$ ) = EVALHELP(EVAL – ITER( $E(C), x, t - 1$ ),  $i_t, j_t, k_t$ )
  - Suffices to show EVALHELP  $\in$  SIZE( $(m + n) \log m + n$ )

$$\text{Temp}(k_t) \leftarrow \text{NAND}(\text{Temp}(i_t), \text{Temp}(j_t))$$

# Sketch of EVALHELP

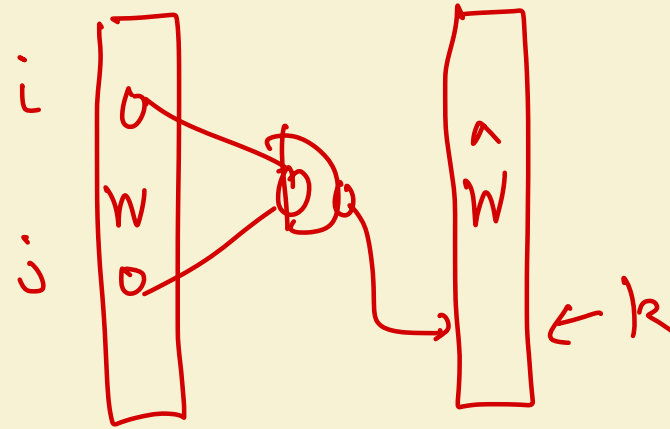

- Key Ingredients:

- $\text{LOOKUP}(W, i) = W_i$  where  $W = W_0 \dots W_{m-1} \in \{0,1\}^m$ ,  $i \in [m]$  represented in binary.

- $\text{UPDATE}(W, k, b) = \widehat{W}$  where  $\widehat{W}_k = b$  and  $\widehat{W}_\ell = W_\ell$  for  $\ell \neq k$

- Claims:

- $\text{LOOKUP} \in \text{SIZE}(m)$
- Exercise:  $\text{UPDATE} \in \text{SIZE}(m^2)$  (even better  $\text{SIZE}(m \log m)$ )
  - Don't have to work out details. Think of the high-level plan.

- $\text{EVALHELP}(W, i, j, k) = \text{UPDATE}\left(W, k, \text{NAND}(\text{LOOKUP}(W, i), \text{LOOKUP}(W, j))\right)$



# Exercise Break 2:

- $\text{UPDATE}(W, k, b) = \widehat{W}$  where  $\widehat{W}_k = b$  and  $\widehat{W}_\ell = W_\ell$  for  $\ell \neq k$

$W, \widehat{W} \in \{0,1\}^m, k \in [m]$  represented in binary

- Exercise:
  - Show  $\text{UPDATE} \in \text{SIZE}(m^2)$  (even better  $\text{SIZE}(m \log m)$ )
    - Don't have to work out details. Think of the high-level plan.

Note that  $UPDATE(W, R, b)_i = b$  if  $R = i$   
 $= W_i$  if  $R \neq i$

Write  $R = R_0 \dots R_\ell$  where  $\ell = \log(m+n)$   
so that  $R = R_0 + 2R_1 + \dots + 2^\ell R_\ell$ .

Similarly  $i = i_0 \dots i_\ell$   
let

then  $UPDATE(W, R, b)_i = IF(\delta_i(R_0 \dots R_\ell), b, W_i)$

where  $\delta_i(R_0 \dots R_\ell) = \text{AND}_{j=0}^{\ell} [NOT(XOR(i_j, R_j))]$

- $\delta_i$  requires  $O(\ell)$  gates;  
 $UPDATE(W, R, b)_i$  also requires  $O(\ell)$  gates  $\Rightarrow UPDATE$  requires  $O(m\ell) = O(m \log m)$  gates

# Circuits: What you need to know

**Theorem I:** Every function  $f: \{0,1\}^n \rightarrow \{0,1\}$  can be computed by circuit of size  $O(2^n/n)$ .



**Theorem II:** Some functions  $f: \{0,1\}^n \rightarrow \{0,1\}$  cannot be computed by circuits of size  $o(2^n/n)$ .



**SIZE Hierarchy Theorem: Book + Section/HW**

**Thm 5.11:**  $\exists C$  ( $C = 1000$  will do) .s.t  $\forall s < \frac{2^n}{Cn}$ ,  $SIZE_{n,1}(s) \subsetneq SIZE_{n,1}(C \cdot s)$

\* If  $f$  outputs  $m$  bits then add factor  $m$  to Thm I,II

# Extended Church Turing Thesis (circuit version)



If  $f: \{0,1\}^n \rightarrow \{0,1\}^m$  can be computed in the physical world using  $s$  resources then  $f$  can be computed by circuit of  $\approx s$  (e.g.  $O(s^2)$  or  $O(s^3)$ ) gates.

*(finite function version – we'll see unbounded function version soon)*


**TL;DR:** So far still stands. Only serious challenge is *quantum computing* ~~which we'll see later.~~

**Non-serious challenges:** *(Following slides stolen from Boaz Barak who stole it from Scott Aaronson)*


# Soap Bubble Computer

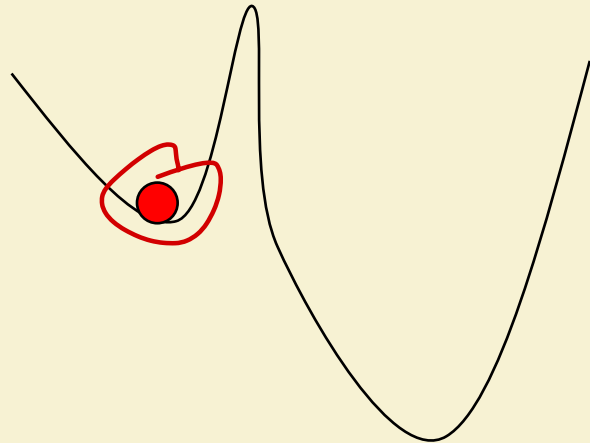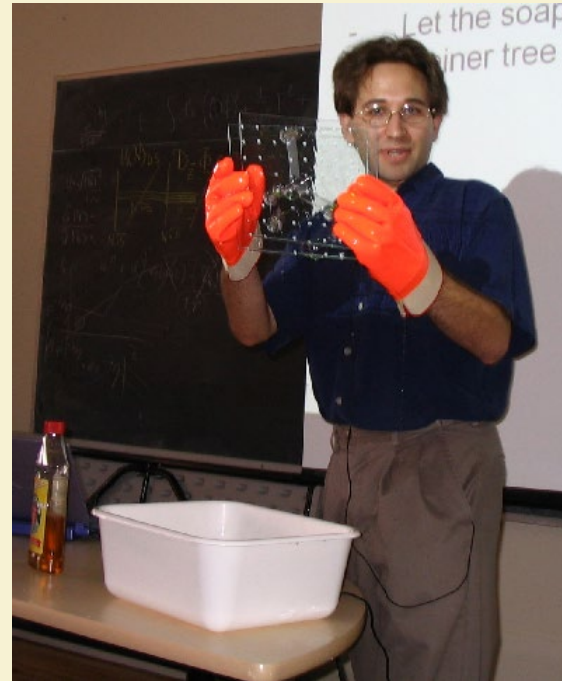

# Protein Folding

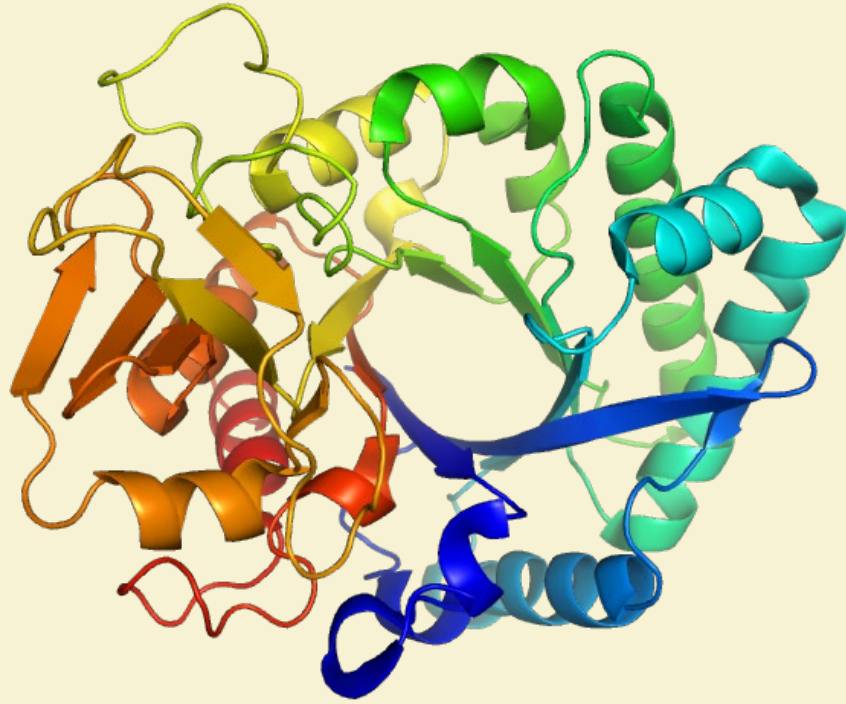


# Spaghetti Sort

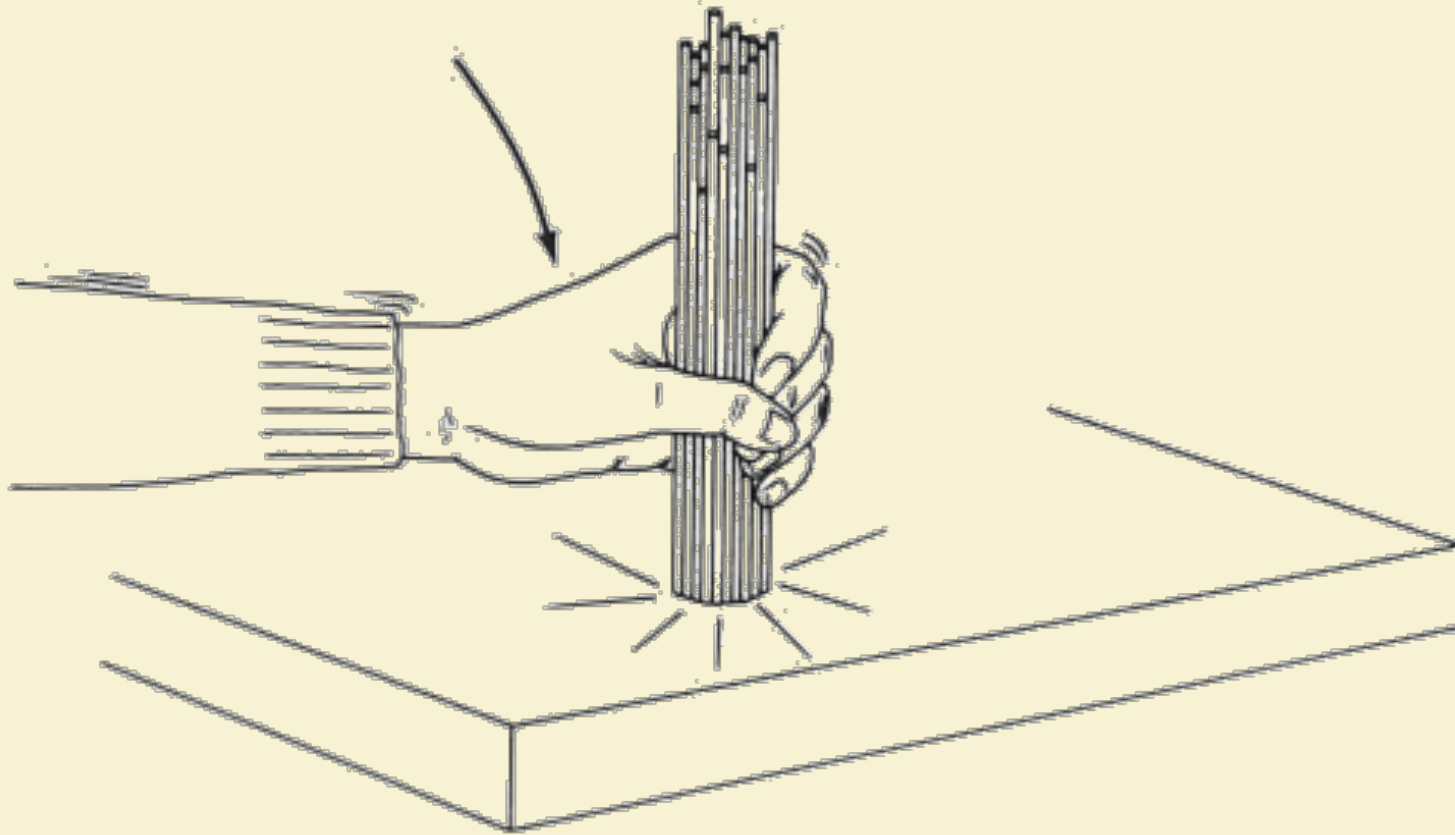



# Relativity Computer

(cf. Malament and Hogarth)

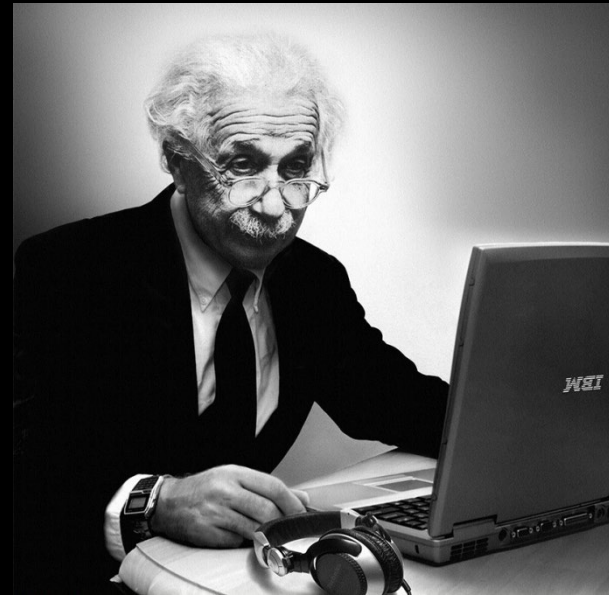





# Zeno's Computer

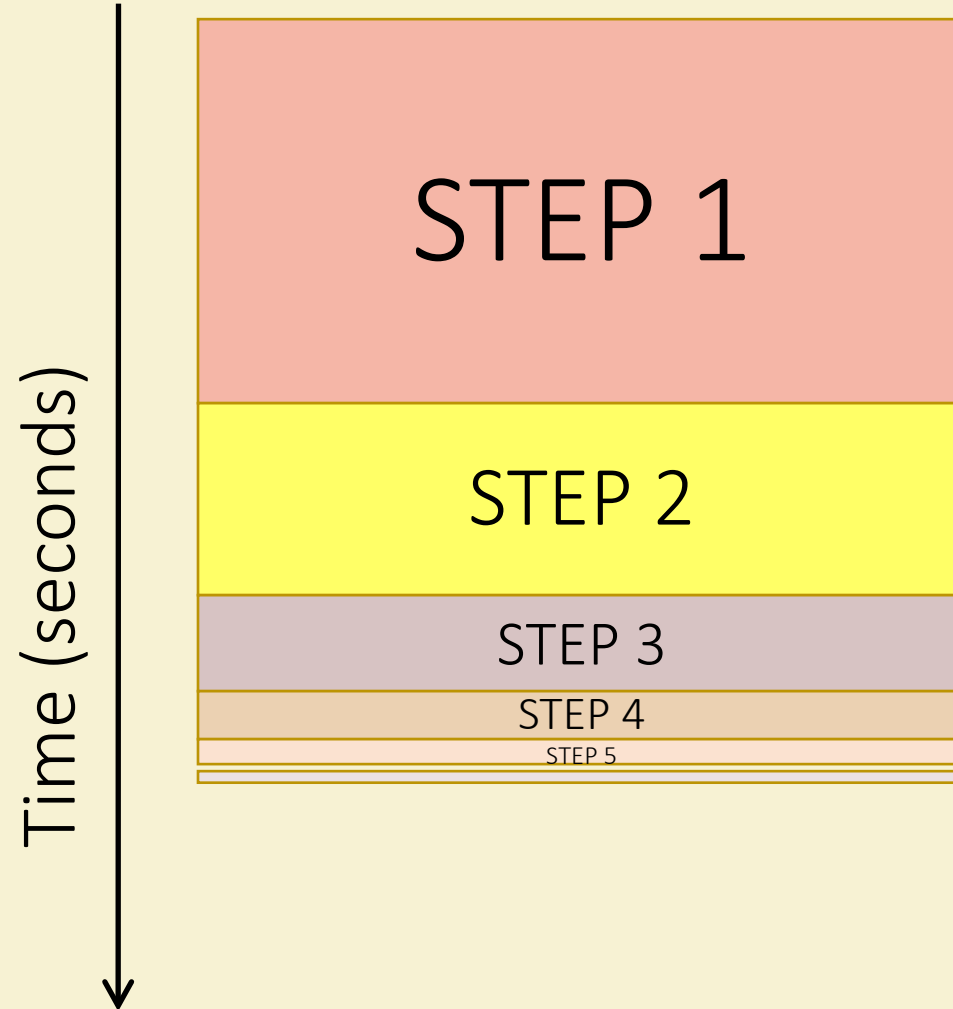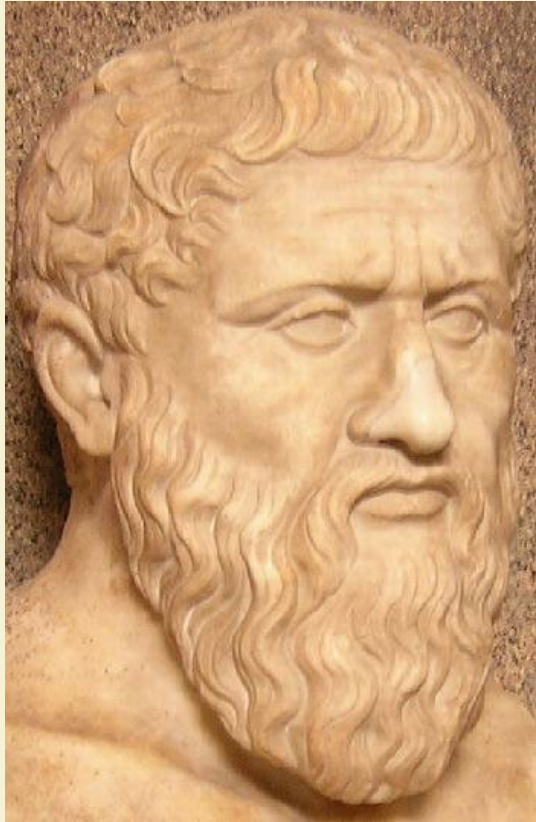

# Where we are:

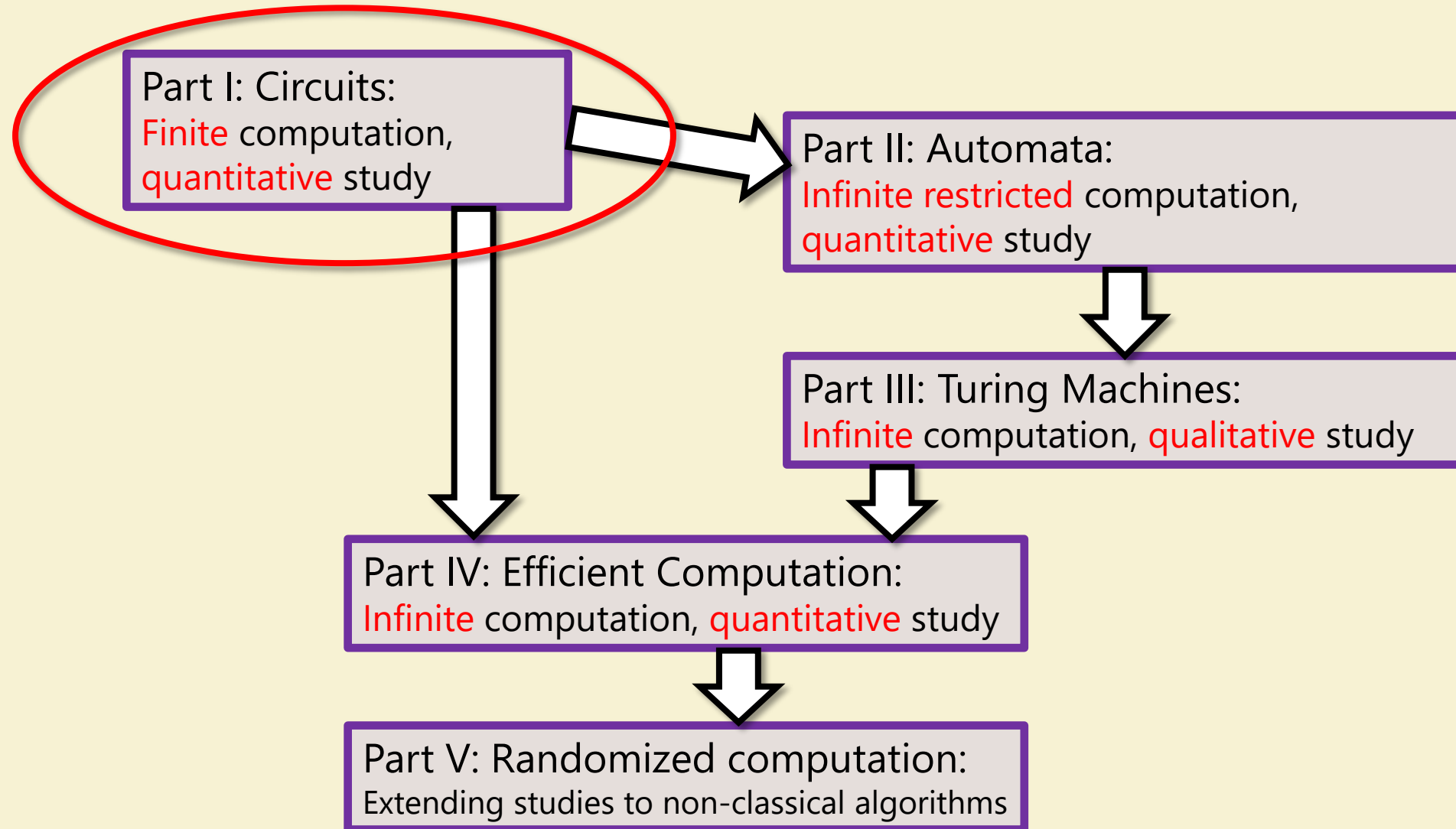

# Where we are:

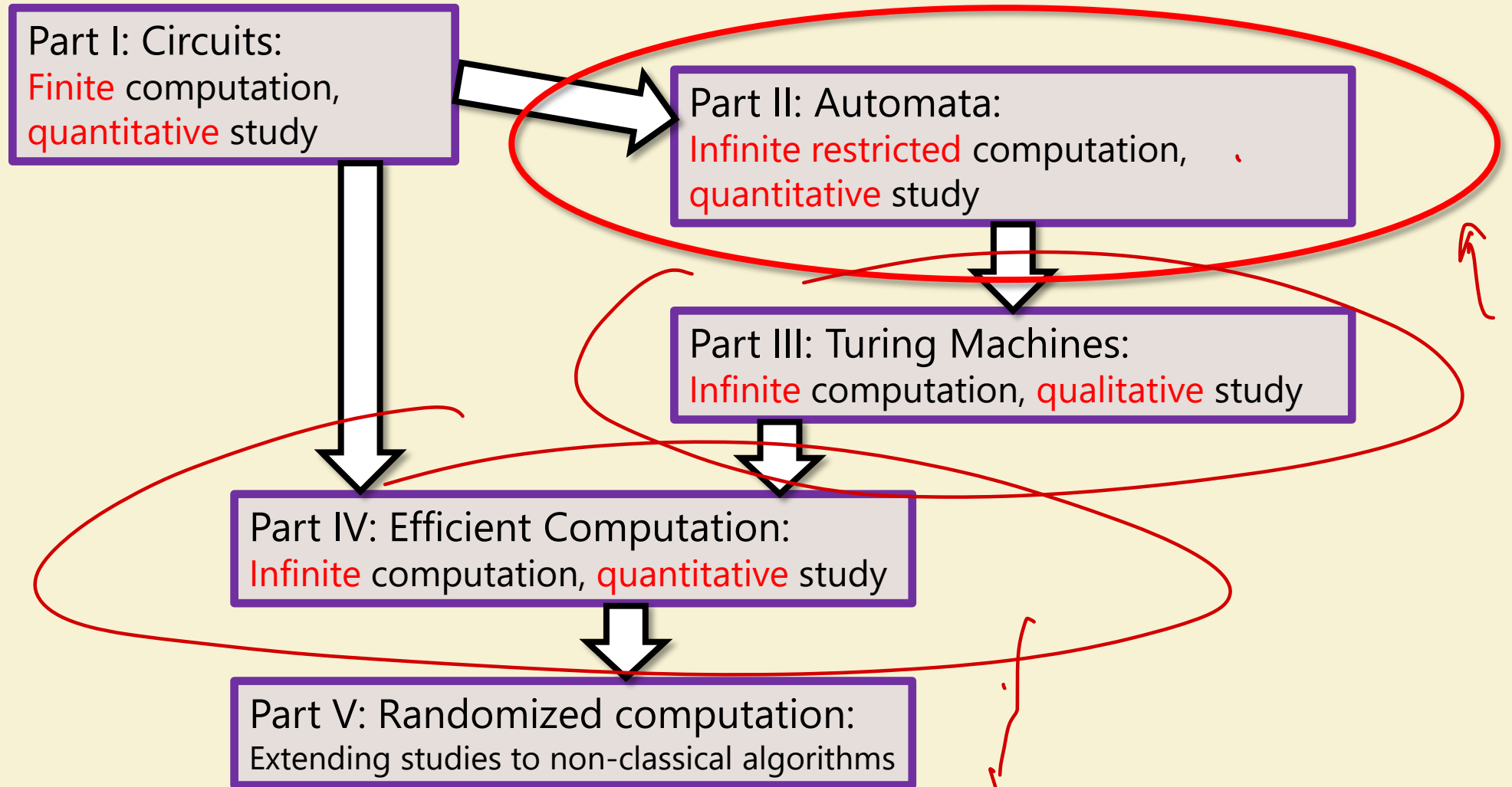

End of Lecture

# If eligible, Get Ready to Vote

- Today is National Voter Registration and Request your Ballot Day
- This year, young people are the largest voting bloc in the country.
  - Less than 50% of Harvard students voted in 2018.
- Visit [bit.ly/HVCpledge](https://bit.ly/HVCpledge). If eligible, make sure to check your voter registration (and make sure that the right addresses are listed) and either request a mail ballot or make a plan to vote in person.
- If you have already completed these steps, still fill out the form to double check! Sometimes people think they are registered when they're not! Not everyone is eligible to vote - encourage your friends to turn out and take action in other ways.
- Questions? Email [voteschallenge@harvard.edu](mailto:voteschallenge@harvard.edu)!